

Name: \_\_\_\_\_

Date: \_\_\_\_\_

## Practice: Circuit Diagrams

### Learning Goals

1. I can use proper symbols when drawing circuits.
2. I can draw a circuit diagram that represents a real circuit.

### Legend



Light bulb



Voltmeter



Battery (greater than 4.5V)



Open switch






Ammeter



Resistor

Draw each of the following circuits into a proper circuit diagram. *Write in pencil!*

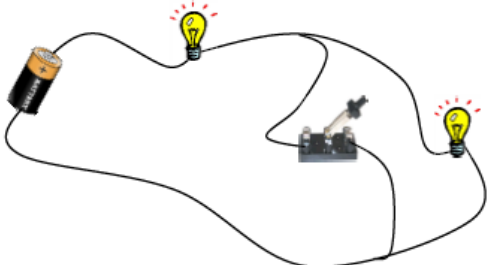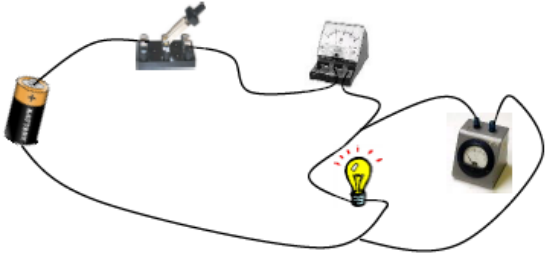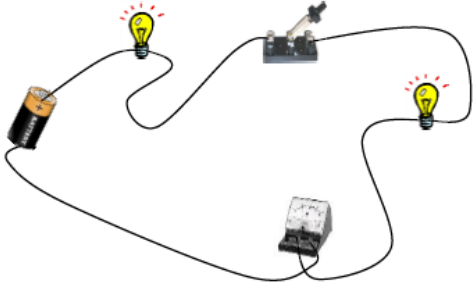Circuit	Circuit Diagram
	
	
	

Name: \_\_\_\_\_

Date: \_\_\_\_\_

