

Name: Solutions







Date: _____

Practice: Circuit Diagrams







Learning Goals

1. I can use proper symbols when drawing circuits.
2. I can draw a circuit diagram that represents a real circuit.

Legend

	Light bulb		Voltmeter		Battery (greater than 4.5V)
	Open switch		Ammeter		Resistor

Draw each of the following circuits into a proper circuit diagram. *Write in pencil!*

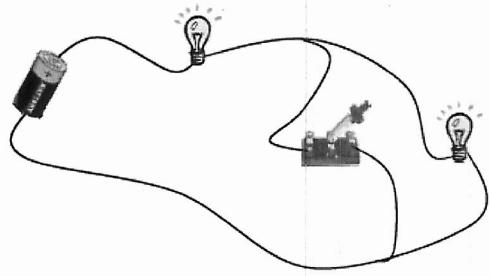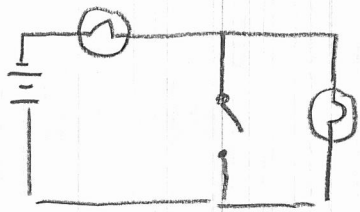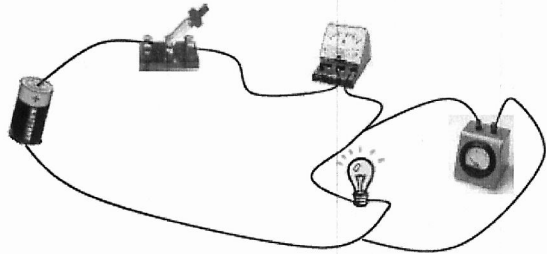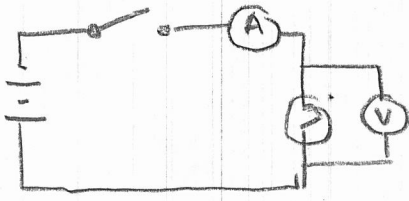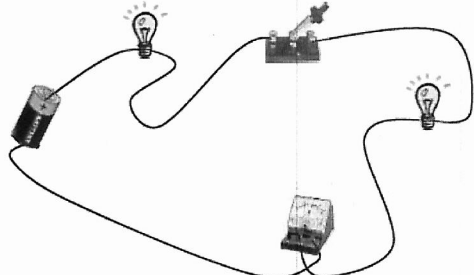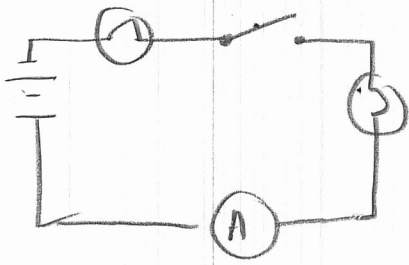Circuit	Circuit Diagram
	
	
	

Name: _____

Date: _____

